CBSE 12 Physics
Module 4
Ch 3 Current
Electricity Part I

Anand Balaraman

Electric Charges Electric

Electric Potenti:

Ohm's Law

Electrical

Solved Examples &

EMF and

Solved Examples &

# CBSE 12 - Physics Module 4 Ch 3 Current Electricity - Part I

#### **Anand Balaraman**

Delhi Public School - Bangalore East

June 22, 2021

### Learning Objectives & Outcomes

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Lav

Electrical Resistance

Solved Examples & Homework

EMF and Terminal PI **Learning Objective**: Objective is to familiarise the learner with the concept of **Electric Current** 

**Learning Outcome**: Upon successful completion of this module, the learner should be able to:

- Describe the motion of electric charges and define Electric Current.
- Define the terms electric current and electric potential
- State the Ohm's Law on electric current and electric potential,
- Distinguish between Ohmic resistors and Non-Ohmic resistors
- Draw the V-I graph for Ohmic and Non-Ohmic resistors.
- List the factors that determine the resistance of a resistor.

### Presentation Outline

CBSE 12 -Physics Module 4 Ch 3 Current Electricity -

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Lav

Electrical Resistance

Solved Examples & Homework

EMF and Terminal PI Electric Charges - Electric Current

2 Electric Potential

3 Ohm's Law

4 Electrical Resistance

5 Solved Examples & Homework

6 EMF and Terminal PD

Solved Examples & Homework

### **Electric Charges - Electric Current**

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Lav

Electrical Resistance

Solved Examples & Homework

EMF and Terminal PD

Solved Examples & **Electric Current**: When an external electric field is applied, positive charges drift along the direction of electric field and negative charges drift against the direction of electric field. The charges in motion constitute electric current.

#### Electric Current

Electric Current is defined as the rate of flow of charge.

$$I = Q/t$$
 : for steady flow;

$$I(t) = \lim_{\Delta t \to 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$
 : for non-steady flow

The SI unit of electric current is ampere (A).

$$1A \equiv \frac{1C}{1s} = 1C.s^{-1}$$

$$1mA = 10^{-3}A;$$
  $1\mu A = 10^{-6}A$ 

### **Charge Carriers - Conventional Current**

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

Anand Balaraman

Electric Charges Electric Current

Potentia

Ohm's Lav

Electrical Resistanc

Solved Examples & Homework

EMF and Terminal PE

Solved Examples &

#### **Charge Carriers:**

- Electric current is the flow of electric charges. But these electric charges are carried by particles like **electrons** and **ionised atoms**.
- In metals, the charge carriers are negatively charged free electrons; In electrolytes and plasma the charge carriers are positively charged **cations** and negatively charged **anions**,
- If 'n' electrons pass through a cross-section in time 't', then total charge passed through the conductor and the electric current are given as:

$$Q = n \times e; \qquad I = \frac{Q}{t} = \frac{ne}{t}$$

• In an electrolyte if  $n_1$  cations, each carrying a charge of  $+q_1$  move in one direction and  $n_2$  anions, each carrying a charge of  $-q_2$  move in opposite direction in time t, the total electric current is:

$$I = \frac{n_1 q_1 + n_2 q_2}{t}$$

EMF and Terminal Pl • In a conductor  $6.25 \times 10^{16}$  electrons flow from one end to another in 2s. The fundamental unit of charge is given as  $e = 1.6 \times 10^{-19} C$ . What is the electric current?

$$I = \frac{Q}{t} = \frac{ne}{t} = \frac{(6.25 \times 10^{16})(1.6 \times 10^{-19}C)}{2s}$$
$$= 5.0 \times 10^{-3}A = 5.0 \, mA$$

② A current of  $1.6\,mA$  flows through a conductor. Find the number of electrons passing through the cross-section each second.

$$I = \frac{Q}{t} = \frac{ne}{t}$$
 
$$n = \frac{I.t}{e} = \frac{(1.6 \times 10^{-3} A)(1s)}{1.6 \times 10^{-19} C} = 10^{16} \text{electrons}$$

### **Charge Carriers - Conventional Current**

CBSE 12 -Physics Module 4 Ch 3 Current Electricity -Part I

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Lav

Electrical Resistance

Solved Examples & Homework

EMF and Terminal PI

Homework

#### Conventional Current:

- Though there is a direction for the flow of charge, this direction information is not usually useful. Often, what is of interest is the rate of flow. Therefore current is considered as a scalar quantity.
- Moreover, negative charges moving in a certain direction have the same effect as positive charges of same magnitude moving in opposite direction.
- Even if the electric current is due to the motion of electrons, the electronic current can be represented as a flow of positive charges in the opposite direction. This abstract representation of electric current by apparent positive charges is called as conventional current.

### Presentation Outline

Anand Balaraman

2 Electric Potential

Solved Examples & Homework

#### **Electric Potential**

CBSE 12 -Physics Module 4 Ch 3 Current Electricity -

Anand Balaraman

Electric Charges Electric Current

Potentia

Ohm's Law

Electrical Resistance

Solved Examples & Homework

EMF and Terminal Pf

Solved Examples &


#### **Electric Potential:**

- Because charges interact, some work has to be done in moving a charge in the vicinity of other charges,
- Electric potential at a given point in space is a measure of the capacity of a charge placed at that point to do work.

#### Electric Potential - Definition

The electric potential at a point in space is defined as the amount of work done per unit charge in bringing a positive "test charge" from infinity (far away) to that point.

$$V = \frac{W}{Q}$$

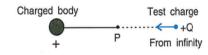



#### **Electric Potential**

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity Part I

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Lav

Electrical Resistanc

Solved Examples & Homework

EMF and Terminal PE

Solved Examples &

#### **Unit of Electric Potential:**

 If 'W' is the work done in bringing a "test charge" from infinity to to the point P, then the electric potential 'V' at that point is given as:

$$V = \frac{W}{Q}$$

The SI unit of electric potential is volt (V):

$$1V \equiv \frac{1J}{1C} = V.C^{-1}$$

#### Definition of Volt

The electric potential at a point is defined as  $1\ V$  when  $1\ J$  of work is done to bring a charge of  $1\ C$  from infinity (far away) to that point.

EMF and Terminal PE

Solved Examples &

#### Electric Potential Difference:

- In practice, we consider the flow of current between two points separated by a finite distance. Therefore, it is sufficient to know the potential difference between those two points,
- If  ${}^{\prime}W_{AB}{}^{\prime}$  is the work done in moving a "test charge" between the points **A** and **B**, then the electric potential difference between the points is given as :

$$\Delta V_{AB} = V_A - V_B = \frac{W_{AB}}{Q}$$

#### Definition of Potential Difference

The electric potential difference between two points in space is equal to the work done per unit charge in moving a "test charge" between the points.

### Presentation Outline

Anand Balaraman

Ohm's Law

Solved Examples & Homework

#### Ohm's Law

Anand **Balaraman** 

• Imagine a conductor through which a current I flows when a potential difference (voltage) V is maintained across it.

 In 1828 Georg Simon Ohm discovered an empirical relation relating I and V

#### Ohm's Law

The current through a conductor is directly proportional to the potential difference (voltage) across it.

$$V \propto I; \Longrightarrow V = RI$$

The constant of proportionality R is called the **Resistance** of the conductor.

• Ohm's Law is not applicable for all materials. It is applicable only for conductors when the current through them is small.

## Ohmic Resistors (V-I graph)

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Law

Electrical Resistance


Solved Examples & Homework


EMF and Terminal PF

Solved

• When Ohm's Law is applicable (R is a constant), the graph of Voltage (V) Vs Current (I) will be a straight line.

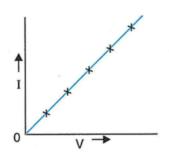• The slope of the V-I graph is the resistance of the conductor.



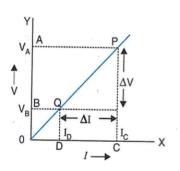

### Ohmic Resistors (V-I graph)

CBSE 12 -Physics Module 4 Ch 3 Current Electricity -

Anand Balaraman

Electric Charges Electric

Electric Potentia

Ohm's Law


Electrical Resistance


Solved Examples & Homework

EMF and

Solved

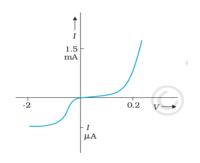• When Ohm's Law is not applicable (non-ohmic resistors), the V-I graph is not a straight line.



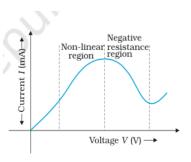

### Presentation Outline

Anand Balaraman

4 Electrical Resistance

Solved Examples & Homework

6 EMF and Terminal PD

### Factors affecting the resistance

Anand **Balaraman** 

#### Factors affecting the resistance (R):

- **1 Length** (*l*): Resistance is directly proportional to the length of the conductor.
- **2** Cross Sectional Area (A): Resistance is inversely proportional to the cross-sectional area of the conductor.
- **3** Resistivity ( $\rho$ ): Resistivity is a material property.

$$R = \rho \frac{l}{A}$$

SI units of **resistance** (R) is  $\Omega$  (pronounced **Ohm**) SI unit of **resistivity** ( $\rho$ ) is  $\Omega - m$ 

#### Combination of Resistors

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

#### Anand Balaraman

Electric Charges Electric Current

Electric Potenti:


Ohm's Law

Electrical Resistance

Solved Examples & Homework

EMF and Terminal PD

Solved Examples &

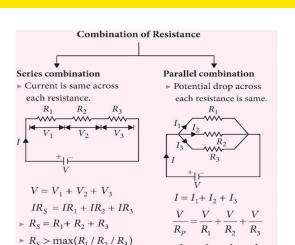

 $R_p < \min(R_1 / R_2 / R_3)$ 

### **Current Branching Rule**


Anand Balaraman

• A current I branches into  $I_1$ through  $R_1$  and  $I_2$  through  $R_2$ :

• The current branching rule is as follows:

$$I_1 = \left(\frac{R_2}{R_1 + R_2}\right)I$$
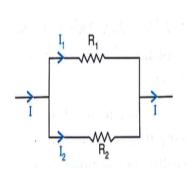
$$I_2 = \left(\frac{R_1}{R_1 + R_2}\right)I$$



### **Voltage Division Rule**


#### Anand Balaraman

• A volatge V is divided into  $V_1$ across  $R_1$  and  $V_2$  across  $R_2$ , connected in series:

• The voltage division rule is as follows:

$$V_1 = \left(\frac{R_1}{R_1 + R_2}\right) V$$
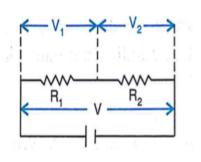
$$V_2 = \left(\frac{R_2}{R_1 + R_2}\right) V$$



### Presentation Outline

Anand Balaraman

Solved Examples & Homework

### Solved Examples

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

Anand Balaraman

Electric Charges Electric

Electric Potentia

Ohm's Law


Electrical Resistanc

Solved Examples & Homework

EMF and Terminal PD

Solved
Examples &

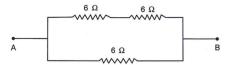Find the equivalent resistances between points A and B.



#### **Solution**

$$R_{tot} = \left(\frac{1}{6\Omega + 6\Omega} + \frac{1}{6\Omega}\right)^{-1}$$
$$= \left(\frac{1}{12\Omega} + \frac{1}{6\Omega}\right)^{-1} = 4\Omega$$

### Solved Examples

CBSE 12 -Physics Module 4 Ch 3 Current Electricity -

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Law


Electrical Resistanc

Solved Examples & Homework

EMF and Terminal PF

Solved

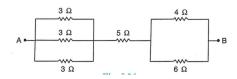2 Find the equivalent resistances between points A and B.



#### Solution

$$R_{tot} = \left(\frac{1}{3\Omega} + \frac{1}{3\Omega} + \frac{1}{3\Omega}\right)^{-1} + 5\Omega + \left(\frac{1}{4\Omega} + \frac{1}{6\Omega}\right)^{-1}$$
$$= 1\Omega + 5\Omega + 2.4\Omega = 8.4\Omega$$

### Homework

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

Anand Balaraman

Electric Charges Electric

Electric Potential

Ohm's Lav

Electrical Resistance

Solved Examples & Homework

EMF and Terminal PE

Solved Examples &

- Answer the following DC circuit related questions :
  - (a) Find the equivalent resistance between points a and b
    in Figure 1a
  - (b) In Figure 1b, if the current through the  $20\,\Omega$  resistor is  $2.0\,\mathrm{A}$ , what is the current I through the  $5\,\Omega$  resistor?

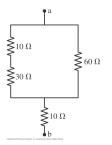


Figure: 1a.

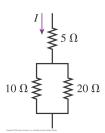


Figure: 1b.

#### Homework

CBSE 12 -Physics Module 4 Ch 3 Current Electricity -

Anand Balaraman

Electric Charges Electric Current

Electric Potentia

Ohm's Lav

Electrical Resistanc

Solved Examples & Homework

EMF and Terminal PE

Solved Examples &

- 2 In the circuit shown in Figure 2, the voltage across the  $2.0\,\Omega$  resistor is  $12\,V.$ 
  - (a) What is the voltage across the  $1.0 \Omega$  resistor?
  - (b) What is the **emf** of the battery
  - (c) What is the total current through the circuit?
  - (d) What is the current through the  $6.0\,\Omega$  resistor?

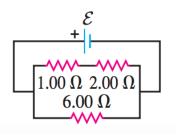


Figure: 2

### Thank You!

CBSE 12 Physics
Module 4
Ch 3 Current
Electricity -

Anand Balaraman

Electric Charges Electric Current

Electric Potenti

Ohm's Lav

Electrical Resistanc

Solved Examples & Homework

EMF and Terminal P

Solved Examples &



### Thank You!